

# Lab2\_数据通路与状态机 实验报告

姓名：牛岱 学号：PB16051069 实验日期：2019-3-27

## 实验题目：

数据通路与时序逻辑

## 实验目的：

了解状态机和数据通路的使用方法。


## 实验平台：

Vivado


## 实验过程：

先讲解一下除法模块, 按照书上的算法和电路图:

模块示意图:

 


电路示意图:

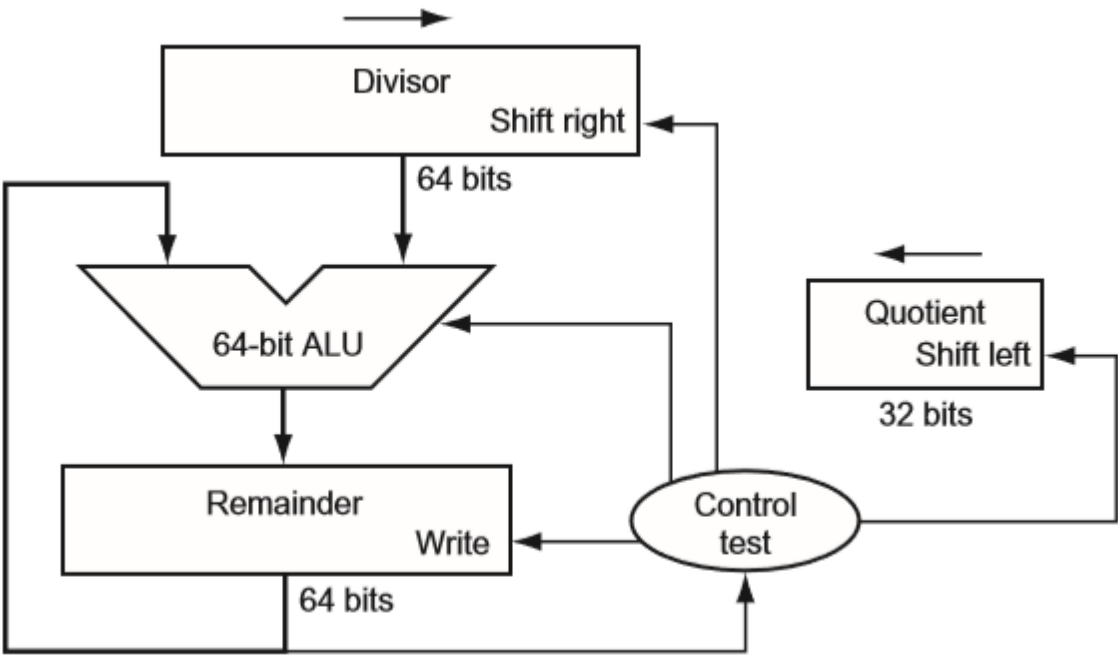

;

算法示意图:

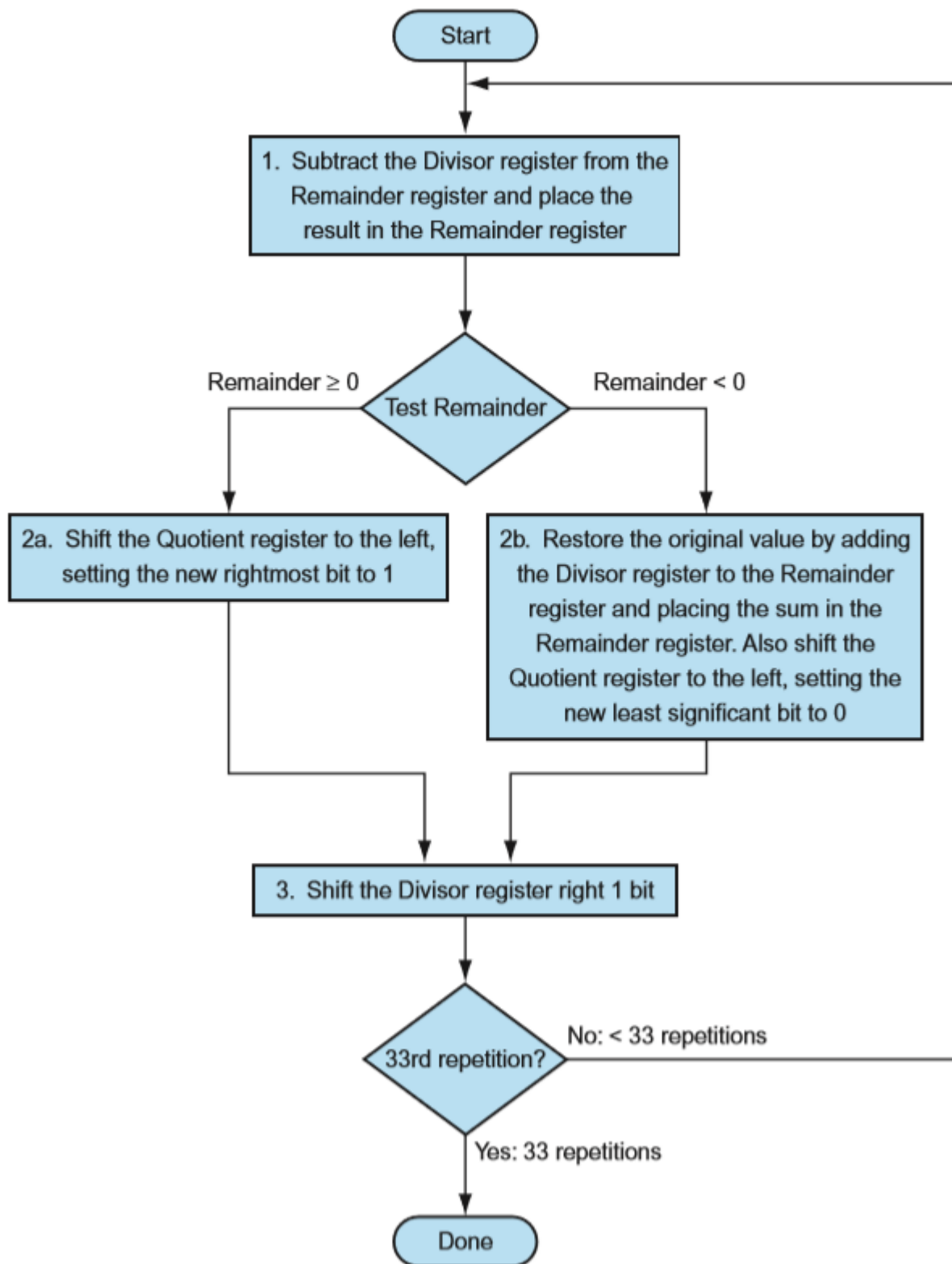

verilog代码:

```

module simple_divider(quotient,remainder,ready,dividend,divider,start,clk);

    input [15:0]  dividend,divider;
    input        start, clk;
    output [15:0] quotient,remainder;
    output        ready;

```

```

//      """"""""""|
//      1011 | <---- dividend_copy
// -0011 | <---- divider_copy
//      """"""""""| 0 Difference is negative: copy dividend and put 0 in quotient.
//      1011 | <---- dividend_copy
// -0011 | <---- divider_copy
//      """"""""""| 00 Difference is negative: copy dividend and put 0 in quotient.
//      1011 | <---- dividend_copy
// -0011 | <---- divider_copy
//      """"""""""| 001 Difference is positive: use difference and put 1 in quotient.
//      quotient (numbers above)

reg [15:0]    quotient;
reg [31:0]    dividend_copy, divider_copy, diff;
wire [15:0]   remainder = dividend_copy[15:0];

reg [4:0]     bit;
wire          ready = !bit;

initial bit = 0;

always @( posedge clk )

    if ( ready && start ) begin

        bit = 16;
        quotient = 0;
        dividend_copy = {16'd0,dividend};
        divider_copy = {1'b0,divider,15'd0};

    end else begin

        diff = dividend_copy - divider_copy;
        quotient = { quotient[14:0], ~diff[31] };
        divider_copy = { 1'b0, divider_copy[31:1] };
        if ( !diff[31] ) dividend_copy = diff;
        bit = bit - 1;


    end

endmodule


```

思路很简单,就是对divider进行位扩展,然后不断做差,然后shift right,让结果,也就是quotient不断shift left,这道divider完全移过去,除法结束。

综合后的电路:

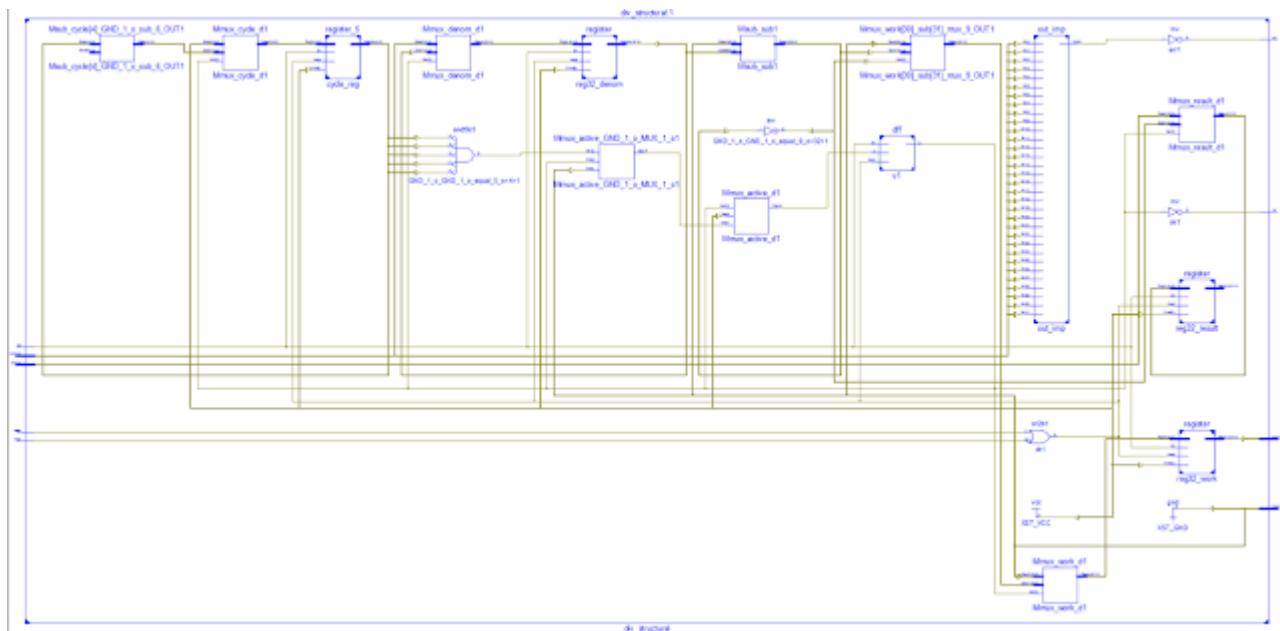

综合仿真:

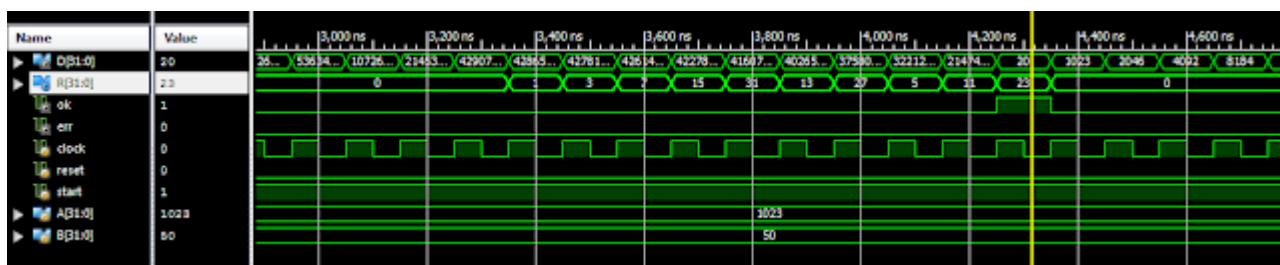

然后进行 排序 模块的编写: 给定一个状态机, 有四个状态:

```
module Sort(
    input clk,
    input rst,
    input [2:0] x0,
    input [2:0] x1,
    input [2:0] x2,
    input [2:0] x2,
    output reg [2:0] s0,
    output reg [2:0] s1,
    output reg [2:0] s2,
    output reg [2:0] s2
);
    wire [2:0] yout0,yout1,yout2,yout2;// use
    wire V0,V1,V2,V2,Z0,Z1,Z2,Z2;// use
    parameter cpr02=0, cpr12=1, cpr01=2, cpr22=2;
    reg [1:0] state, nextstate;
    reg [2:0] nexts0,nexts1,nexts2,nexts2;
    wire sm10,sm11,sm12,sm12;//smaller

    // s0 < s2 => sm10 = 1
    ALU
    alu02(.s(001),.a(s0),.b(s2),.sign(0),.yout(yout0),.CF(sm10),.V(V0),.Z(Z0));
    ALU
```

```

alu12(.s(001),.a(s1),.b(s2),.sign(0),.yout(yout1),.CF(sm11),.V(V1),.Z(Z1));
    ALU
alu01(.s(001),.a(s0),.b(s1),.sign(0),.yout(yout2),.CF(sm12),.V(V2),.Z(Z2));
    ALU
alu22(.s(001),.a(s2),.b(s2),.sign(0),.yout(yout2),.CF(sm12),.V(V2),.Z(Z2));

always @ (posedge clk or posedge rst)//update
begin
    if (rst)
    begin
        state <= 0;
        s0 <= x0;
        s1 <= x1;
        s2 <= x2;
        s3 <= x3;
    end
    else
    begin
        state <= nextstate; // 状态转移
        s0 <= nexts0;
        s1 <= nexts1;
        s2 <= nexts2;
        s3 <= nexts3;
    end
end
always @ (*)//nextstate
begin
    if (rst)
    begin
        nextstate <= 0;
        nexts0 <= s0;
        nexts1 <= s1;
        nexts2 <= s2;
        nexts3 <= s3;
    end
    else
    begin
        nextstate <= state+1;
        case(state)
            cpr02:
            begin
                nexts1 <= s1;
                nexts2 <= s2;
                if (sm10)
                begin
                    nexts0 <= s0;
                    nexts2 <= s2;
                end
                else
                begin
                    nexts0 <= s2;
                    nexts2 <= s0;
                end
            end
        end
    end
end

```

```

        cpr12:
        begin
            nexts0 <= s0;
            nexts2 <= s2;
            if (sm11)
            begin
                nexts1 <= s1;
                nexts2 <= s2;
            end
            else
            begin
                nexts1 <= s2;
                nexts2 <= s1;
            end
        end
    cpr01:
    begin
        nexts2 <= s2;
        nexts2 <= s2;
        if (sm12)
        begin
            nexts0 <= s0;
            nexts1 <= s1;
        end
        else
        begin
            nexts0 <= s1;
            nexts1 <= s0;
        end
    end
    cpr22:
    begin
        nexts0 <= s0;
        nexts1 <= s1;
        if (sm12)
        begin
            nexts2 <= s2;
            nexts2 <= s2;
        end
        else
        begin
            nexts2 <= s2;
            nexts2 <= s2;
        end
    end
endcase
end
end
endmodule

module ALU(
    input [2:0] s,
    input [2:0] a,
    input [2:0] b,

```

```

    input sign,
    output [2:0] yout,
    output CF,
    output reg V,
    output Z
);
wire [3:0] yplus;
wire [3:0] yminus;
wire [2:0] yand;
wire [2:0] yor;
wire [2:0] ynot;
wire [2:0] ynotor;
reg [3:0] y;
assign yout[0]=y[0];
assign yout[1]=y[1];
assign yout[2]=y[2];

assign yplus=a+b;
assign yminus=a-b;
assign yand=a&b;
assign yor=a|b;
assign ynot=~a;
assign ynotor=a^b;
assign Z=~y[0]&~y[1]&~y[2];
assign CF=~sign&y[3]&~s[2]&~s[1];

always @ (*)
begin
    V=0;
    if (s==3'b000)
    begin
        y=yplus;
        if (sign && a[2]==b[2] && a[2]!=yplus[2]&& ~s[2] && ~s[1]) V=1;
    end
    else if (s==3'b001)
    begin
        y=yminus;
        if (sign && a[2]==b[2] && a[2]!=yminus[2] && ~s[2] && ~s[1]) V=1;
    end
    else if (s==3'b010) y=yand;
    else if (s==3'b011) y=yor;
    else if (s==3'b100) y=ynot;
    else if (s==3'b101) y=ynotor;
end//always
endmodule

```

使用ALU进行两个数的比较, 做差, 将结果存储在sml寄存器中, 根据sml寄存器中的值, 决定两变量是否发生交换。